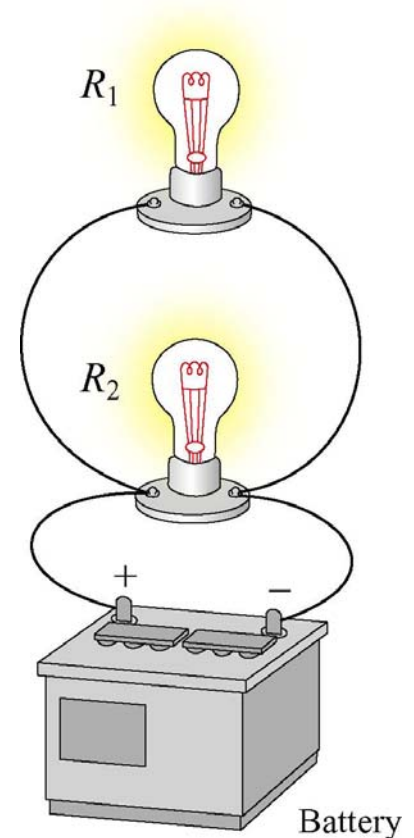



Bulbs and Batteries

An ideal battery is hooked to a light bulb with wires. A second identical light bulb is connected in parallel to the first light bulb. After the second light bulb is connected, the current from the battery compared to when only one bulb was connected.



1. Is Higher
2. Is Lower
3. Is The Same
4. Don't know

Bulbs and Batteries

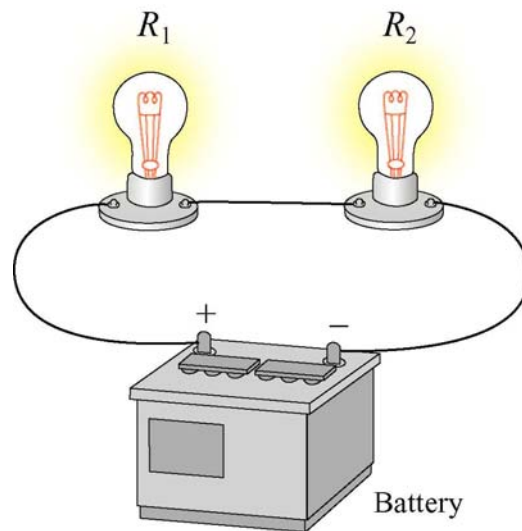


An ideal battery is hooked to a light bulb with wires. A second identical light bulb is connected in series with the first light bulb. After the second light bulb is connected, the current from the battery compared to when only one bulb was connected.

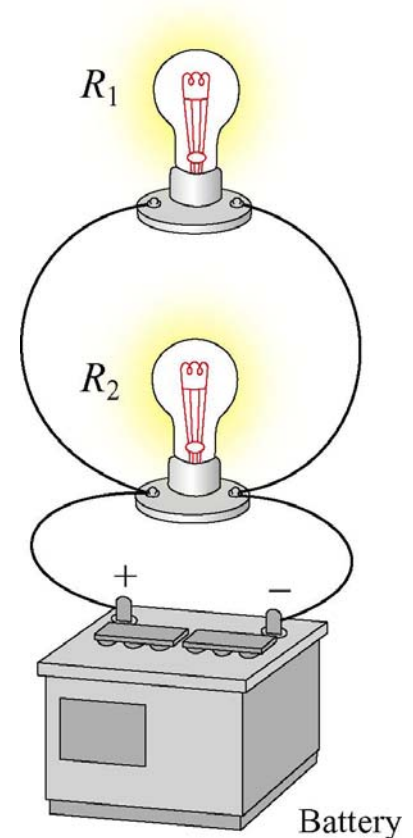1. Is Higher
2. Is Lower
3. Is The Same
4. Don't know


Bulbs and Batteries

An ideal battery is hooked to a light bulb with wires. A second identical light bulb is connected in parallel to the first light bulb. After the second light bulb is connected, the power output from the battery (compared to when only one bulb was connected)



1. Is four times higher
2. Is twice as high
3. Is the same
4. Is half as much
5. Is one quarter as much
6. Don't know

Bulbs and Batteries

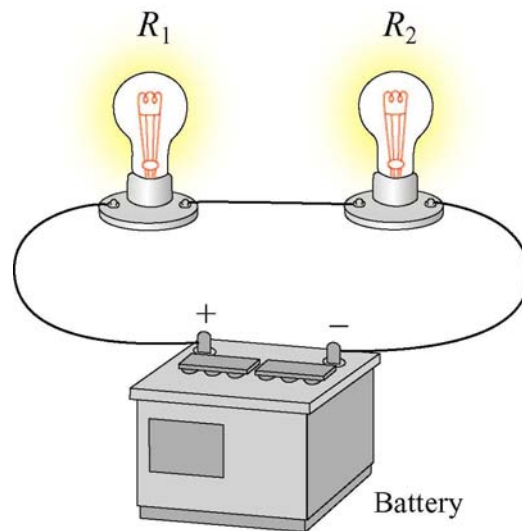

An ideal battery is hooked to a light bulb with wires. A second identical light bulb is connected in series with the first light bulb. After the second light bulb is connected, the light from the first bulb (compared to when only one bulb was connected)

1. is four times as bright
2. is twice as bright
3. is the same
4. is half as bright
5. is one quarter as bright